

# MT EDUCARE LTD.

ICSE X


SUBJECT : **PHYSICS**

**Current Electricity, Household Circuits (Numericals)**

**Assignment Sheet**

**STEP UP ANSWERSHEET**

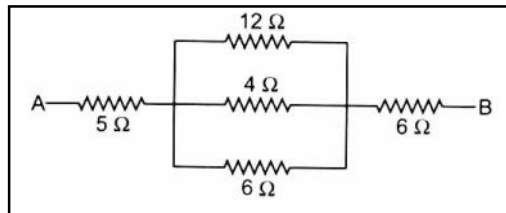26. In the given circuit,  $4\ \Omega$ ,  $4\ \Omega$  and  $4\ \Omega$  in series gives  $R_1 = 4 + 4 + 4 = 12\ \Omega$  and  $2\ \Omega$ ,  $2\ \Omega$  and  $2\ \Omega$  in series gives  $R_2 = 2 + 2 + 2 = 6\ \Omega$ . Now,  $R_1 = 12\ \Omega$ ,  $R_2 = 6\ \Omega$  and  $R_3 = 4\ \Omega$  are in parallel.



The equivalent resistance  $R'$  is given by

$$\begin{aligned}\frac{1}{R'} &= \frac{1}{12} + \frac{1}{4} + \frac{1}{6} \\ &= \frac{1+3+2}{12} = \frac{6}{12}\end{aligned}$$

$$\begin{aligned}\frac{1}{R'} &= \frac{1}{2} \\ R' &= 2\ \Omega\end{aligned}$$



Total resistance =  $5 + 2 + 6 = 13\ \Omega$ .

**(ICSE 2013)**

27. (i) We know,  $V = IR'$   
 $6 = 0.5 \times R'$   
 $R' = 12\ \Omega$   
 $R' = 3 + R$   
 $12 = 3 + R$   
 $R = 9$
- (ii) Charge,  $q = It$   
 $q = 0.5 \times 120 = 60$  coulomb

(iii) Power dissipation,  $P = I^2R$   
 $P = 0.5^2 \times 3 = 0.75\ \text{W}$

**(ICSE 2013)**

28.  $R' = n^2R$   
 $= 2^2 \times 6 = 24\ \Omega$ .

**(ICSE 2013)**

29. **(29 and 31 Same Answer)**

$$\frac{1}{R_1} = \left( \frac{1}{3} + \frac{1}{3} + \frac{1}{3} \right)$$

$$\Rightarrow \frac{1}{R_1} = 1$$

$$\Rightarrow R_1 = 1\Omega$$

$$R_2 = 5\Omega$$

$$\frac{1}{R_3} = \frac{1}{4} + \frac{1}{6} = \frac{10}{24}$$

$$\Rightarrow R_3 = \frac{24}{10}\Omega$$

$\therefore$  Equivalent resistance can be calculated as,


$$R_{eq.} = R_1 + R_2 + R_3$$

$$= 1 + 5 + \frac{24}{10}$$

$$R = 8.4\Omega$$

(ICSE 2014)

30. (30 and 32 Same Answer)

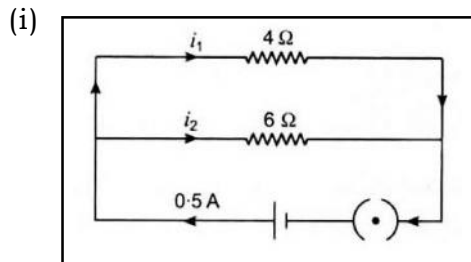

(ii)  $\frac{1}{R} = \frac{1}{4} + \frac{1}{6}$

$$R = 2.4\Omega$$

Now,

$$V = IR$$


$$V = 0.5 \times 2.4 = 1.2V$$

$$i_1 = \frac{V}{R_1} = \frac{1.2}{4} = 0.3A$$

$$i_2 = \frac{1.2}{6} = 0.2A$$

(ICSE 2014)

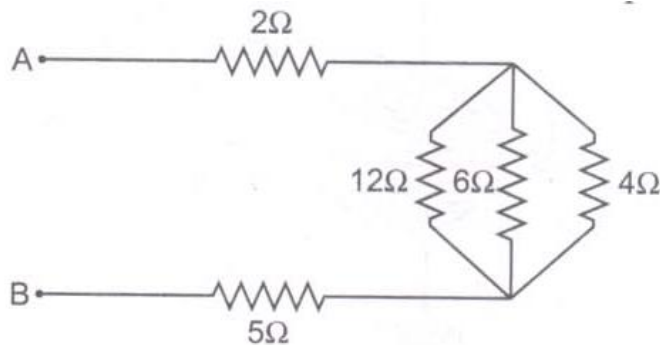33. Three resistance  $12\Omega$ ,  $6\Omega$  and  $4\Omega$  are combined in parallel.




The equivalent resistance in parallel is given by

$$\frac{1}{R_p} = \frac{1}{12} + \frac{1}{6} + \frac{1}{4}$$

$$\frac{1}{R_p} = \frac{1 + 2 + 3}{12}$$
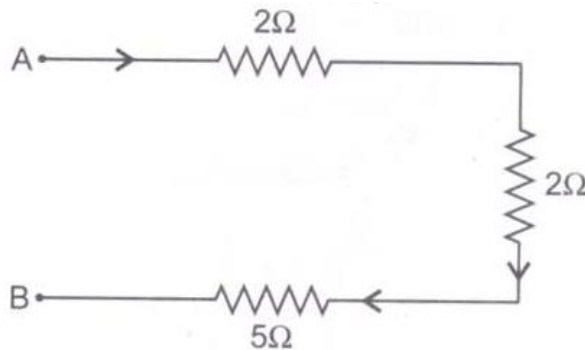
$$\frac{1}{R_p} = \frac{12}{(1 + 2 + 3)} = 2\Omega$$



Now,  $2\Omega$ ,  $R_p$  and  $5\Omega$  are in series.

Thus, the equivalent resistance between A and B =  $2\Omega + 2\Omega + 5\Omega = 9\Omega$

**(ICSE 2015)**

34. The resistance of  $4.5\Omega$  and  $9\Omega$  are connected in parallel  
 $\therefore$  Equivalent resistance,

$$R_1 = \frac{(4.5 \times 9)}{(4.5 + 9)} = \frac{40.5}{13.5} = 3\Omega$$

Total resistance in the circuit (R) =  $1.2 + 0.8 + 3 = 5\Omega$

(i) Current in the circuit (I) = Reading of the ammeter

$$= \frac{\text{Total e.m.f. (E)}}{\text{Total resistance (R)}}$$

$$= \frac{2}{5} \text{ amperes} = 0.4 \text{ ampere}$$

(ii) Potential difference across the terminals of the cell (V)

= total p.d in the external circuit

$$= E - Ir$$

$$= 2 - (0.4 \times 1.2)$$

$$= 2 - 0.48$$

$$= 1.52 \text{ volts}$$

**(ICSE 2015)**

35. Given :  $I = 400 \text{ mA} = 400 \times 10^{-3} \text{ A} = 0.4 \text{ A}$ ,  $V = 12 \text{ V}$

(i) Resistance  $R = \frac{V}{I} = \frac{12}{0.4} = 30\Omega$

(ii) Current drops to  $I = 320 \text{ mA} = 320 \times 10^{-3} \text{ A} = 0.32 \text{ A}$

Now battery voltage  $V = I'R = 0.32 \times 30 = 9.6 \text{ V}$

**(ICSE 2016)**

36. Given :  $R = 20\Omega$ ,  $I = 2.5 \text{ A}$ ,  $t = 5 \text{ min} = 5 \times 60 \text{ s} = 300 \text{ s}$

Heat produced  $H = I^2Rt = (2.5)^2 \times 20 \times 300 = 3.75 \times 10^4 \text{ J}$

**(ICSE 2016)**

37. Given,  $\epsilon = 12 \text{ V}$ ,  $r = 2 \Omega$ ,  $R_A = 4 \Omega$ ,  $R_B = 6 \Omega$ ,  $t = 1 \text{ min} = 60 \text{ s}$

(i) Total resistance of circuit  $R = R_A + R_B + r = 4 + 6 + 2 = 12 \Omega$

Current in the circuit  $I = \frac{\epsilon}{R} = \frac{12\text{V}}{12\Omega} = 1 \text{ A}$

(ii) Terminal voltage of the battery  $V = \epsilon - IR = 12 - 1 \times 2 = 10 \text{ V}$

(iii) p.d. across the resistor B (of  $6 \Omega$ )  $V_B = IR_B = 1 \times 6 = 6 \text{ V}$

(iv) Electrical energy spent in resistor A ( $= 4 \Omega$ )  $= I^2 R_A t$   
 $= (1)^2 \times 4 \times 60 = 240 \text{ J}$

**(ICSE 2016)**

38. Given,  $R = 500 \Omega$ ,  $I = 0.4 \text{ A}$ .

Power of bulb  $P = I^2 R = (0.4)^2 \times 500 = 80 \text{ W}$ .

Potential difference at the ends of the bulb  $V = IR = 0.4 \times 500 = 200 \text{ V}$ .

**(ICSE 2017)**

